

# **Main Board:**

## **Power Tests:**

### **1. TPS54226PWPR (3.3V Voltage Regulator)**

- ☒ ~~Apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply~~
- ☒ ~~Measure output voltage on TPS54226 using a multi~~
- ☒ ~~Result: Output voltage should be 3.3V +/- 0.05V~~

### **2. TPS7A4501DCQT (5V Voltage Regulator)**

- ☒ ~~Apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply~~
- ☒ ~~Measure output voltage on TPS7A4501 using a multimeter in voltage mode across the capacitor (C56)~~
- ☒ ~~Result: Output voltage should be 5V +/- 0.1V~~

### **3. BQ25883RGER (USB Charger)**

- ☒ ~~Disconnect battery terminal (J10) and connect USB cable from PC to mainboard~~
- ☒ ~~Measure voltage across capacitor C29/C37 (VBUS), to be about 5V~~
- ☒ ~~When USB is plugged, it can charge the battery and power the system (3.3V and 5V lines are active)~~

## MCU Tests:

## 1. RP2040 (Main MCU)

- ☒ ~~Connect USB cable from PC to mainboard~~
- ☒ ~~RP2040 appears as USB drive on PC~~

## 2. MR25H40MDF (Flash storage)

- ☒ ~~Install Circuitpython firmware on MCU~~
- ☒ ~~Check size of the MCU USB drive~~
- ☒ ~~Size of drive is 4MB~~

## 3. MAX706RESA+ (Circuit Watch Dog)

### Test 1:

- ☒ ~~Write Circuitpython test script to enable Watch Dog Timer (WDT) by setting the WDT\_EN pin high~~
- ☒ ~~Mainboard resets within 1.6 seconds~~

### Test 2:

- ☒ ~~Write Circuitpython test script to toggle the WDT\_WDI pin between high and low (pulse) every 0.5 seconds~~
- ☒ ~~Set WDT\_EN pin high~~
- ☒ ~~Mainboard should not reset~~

## Device Tests:

## 1. SD Card

- ☒ ~~Measure voltage across capacitor C32/C33, to be 3.3V +/- 0.05V~~
- ☒ ~~Write circuitpython script to establish SPI connection. Script should not return errors.~~
- ☒ ~~RP2040 can successfully read and write data to the card~~

## 2. BNO085 (IMU)

- ☒ ~~Measure voltage across capacitor (C18/C19), to be 3.3V +/- 0.05V~~
- ☒ ~~Write circuitpython script to establish I2C connection. Script should not return errors.~~
- ☒ ~~Accelerometer can respond to linear acceleration changes, and does not return null or invalid values~~
- ☒ ~~Gyroscope can respond to the angular velocity changes and does not return null or invalid values~~
- ☒ ~~Magnetometer can respond to magnetic fields changes and does not return null or invalid values~~

## 3. DS3231S (RTC)

- ☒ ~~Measure voltage across capacitor (C34), to be 3.3V +/- 0.05V~~
- ☒ ~~Write circuitpython script to establish I2C connection. Script should not return errors.~~
- ☒ ~~Write circuitpython script to set RTC to correct time.~~
- ☒ ~~Remove power to the mainboard~~
- ☒ ~~Let RTC remain powered through button cell only for 15 minutes~~
- ☒ ~~Write circuitpython script to check RTC time~~
- ☒ ~~RTC time should be within 1 second of real time~~

# Communications Tests:

## 1. E22-900M30S (LoRa)

- ☒ ~~Write circuitpython script to establish SPI connection. Script should not return errors.~~
- ☒ ~~Set TX\_EN pin high, observe power consumption on DC power supply.~~
- ☐ Power consumption should be under 1W
- ☒ ~~Set RX\_EN pin high, observe power consumption on DC power supply~~
- ☐ Power consumption should be under 0.25W

## 2. S1216V8 (GNSS Receiver)

- ☒ ~~Measure voltage across capacitor (C51?), to be 3.3V +/- 0.05V~~
- ☒ ~~Established UART communication~~

## ~~External Connector~~

### ~~Camera Board~~

- ☐ ~~Proper power connection~~
- ☐ ~~Successful RX/TX transmission~~
- ☐ ~~Successful I2C communication~~
- ☐

### ~~Battery Board~~

- ☐ ~~Proper power connection~~
- ☐ ~~Successful I2C communication~~
- ☐ ~~Successful battery alert signal~~
- ☐

### ~~Jetson Board~~

- ☐ ~~Proper power connection~~
- ☐ ~~Successful I2C communication~~
- ☐ ~~Successful SPI communication~~
- ☐ ~~Proper slave select signal from RP2040~~
- ☐

### ~~XYZ Boards~~

- ☐ ~~Proper power connection~~
- ☐ ~~Successful I2C communication~~

# Battery Board:

## Pre-test procedure:

- Use Power supply as a power source instead of Battery cells
- Apply 2 Power supplies in series (suggest):  
First one 3.7V->left bottom pad-> + (positive)  
->Right up pad-> - (negative)  
Second one 3.7V->Right up pad-> + (positive)  
->Left up pad-> - (negative)

Or

1 Power supply:

7.4V->left bottom pad-> + (positive)  
->Left up pad-> - (negative)

## Power Tests:

### 1. Battery Board 3.3V (from main board)

- ☐ Connect the Mainboard from the port J10
- ☐ Measure output voltage using a multimeter in voltage mode across the capacitor (C16)
- ☐ Result: Output voltage should be 3.3V +/- 0.1V

### 2. Output Power (J7)



- ☐ Measure output voltage using a multimeter in voltage mode (between SYSTEM\_VDD and SYSTEM\_VSS)
- ☐ Result: Output voltage should be 7.4V +/- 0.1V

## Battery Monitor

MAX17205G+

- ☐ The voltage across C6 shall be 3.7 to 4.2V;  
Voltage across C5 shall be 3.7 to 4.2V.
- ☐ MCU can detect its I2C address
- ☐ Proper voltage readings and other information like the State of Charge sent through I2C
- ☐ Send Alert signal once bad things happen

## Battery Bus Protection

- ☐ If the CHARGE\_EN and DISCHARGE\_EN are low, the SYSTEM\_VDD should be approximately equal to the battery voltage (BATT2).
- ☐ CHARGE\_ACTIVE should only be high if charging, and DISCHARGE\_ACTIVE should only be high if the battery discharges.
- ☐ When discharging, the U8 Gate-Ground should be High, the U9 Gate-Ground should be

low. When charging, the U8 Gate-Ground should be low, and the U9 Gate-Ground should be high.

## Battery Temperature Protection

BTS5090-1EJA

- ☐ C18 measures 7.4V.
- ☐ It shall activate and deactivate based on the signal from the IO Expander
- ☐ It shall cut off the current if the temperature exceeds a certain threshold.

Resistor Array

- ☐ Generate enough heat to warm up the batteries
- ☐ The circuit can withstand the heat without damaging itself

## ~~I/O Expander~~

~~PCA9536D~~

- ☐ ~~C16 is Properly powered by 3.3V~~
- ☐ ~~Establish I2C connection and send out proper signals~~

- ☐ ~~While discharging, successfully receive the CHARGE\_ACTIVE and DISCHARGE\_ACTIVE signals from IO0 and IO1~~
- ☐ ~~While discharging, successfully send the HEATER\_ENABLE signals from IO2 and IO3~~

## **Pre-test procedure:**

- Remove the external power source
- Use two 18650 batteries and load them on the battery holder

## **Battery Test:**

- ☐ Measure output voltage using a multimeter in voltage mode
  - 0V at BATT0
  - 3.7V to 4.2V at BATT1
  - 3.7V to 4.2V at BATT2
- ☐ No reverse charging between batteries (Each Battery should have approximately the same voltage)

## **Output Power (J7):**

- ☐ Measure output voltage using a multimeter in voltage mode (between SYSTEM\_VDD and SYSTEM\_VSS)
- ☐ Result: Output voltage should be 7.4V +/- 0.1V

### **Pre-test procedure:**

#### **2 power sources (suggested):**

**One on the pad: left down + / left up -**

**One on J7: SYSTEM\_VDD + / SYSTEM\_VSS -**

### **Battery Bus Detection:**

#### **1. S-8209AAA-T8T1U (Discharge/Over Power Protection)**

- ☐ Change the Pad power source to 8.4V
- ☐ Measure DISCHARGE\_EN voltage using a multimeter in voltage mode, It should be HIGH
- ☐ Measure the voltage between two sides of U4 to see if it is the same

#### **2. S-8209AAA-T8T1U (Changing/Under Power Protection)**

- ☐ Change the Pad power source to 4.8V
- ☐ Measure CHARGE\_EN voltage using a multimeter in voltage mode, It should be HIGH

- ☐ Measure the voltage between two sides of U6 to see if it is the same

### 3. LTC4412xS6 (No need To test)

## Interfaces

#### J10

- ☐ ~~Send out the correct alert signal~~
- ☐ ~~Send proper I2C data~~
- ☐ ~~Send 3.3V power~~

#### J7

- ☐ ~~Send out the correct VDD power~~

#### J8

- ☐ ~~Send out the correct alert signal~~
- ☐ ~~Send proper I2C data~~
- ☐ ~~Send 3.3V power~~

# **X/Y Board:**

## **Pre-test procedure:**

- ☐ Connect with Deployables with J1, and connect with Mainboard with J2.
- ☐ The mainboard should also connect to the Batteryboard and follow the pre-test procedure of the Batteryboard.
- ☐ Deployables should face the sun or artificial sunlight for power generation.

## **Power Tests:**

### **1. DRV8235RTER (Coil Driver)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply.
- ☐ Measure output voltage on DRV8235RTER using a multimeter in voltage mode across the capacitor (C26/C27)
- ☐ Result: Input voltage should be 7.4V  $\pm$  0.1V

### **2. OPT4003DNPRQ1 (Light Sensor)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply.
- ☐ Measure input voltage on OPT4003DNPRQ1 using a multimeter in voltage mode across the capacitor (C36).
- ☐ Result: Input voltage should be 3.3V +/- 0.05V

### **3. LTC3130 (MPPT)**

- ☐ Measure the voltage generated ( $V_{in}$ ) from the deployable using a multimeter in voltage mode across the capacitor (C13-C16).
- ☐ Input voltage between  $V_{in}$  and Ground should be at least higher than 10V as a result of the MPPT.
- ☐ Ideally, the input voltage between  $V_{in}$  and Ground should be about 16V as a result of the MPPT.
- ☐ Output voltage between  $V_{out}$  and Ground should be higher than 7.4V as a result of FB.

### **4. LTC4412xS6 (Or-ing)**

- ☐ Measure the voltage using a multimeter in voltage mode across the capacitor (C1).

- ☐ Result: Input voltage should be ?V +/- ?V

## **5. ADM1176-1ARMZ-R7 (Power Monitor)**

- ☐ Measure the voltage using a multimeter in voltage mode between R124 and the Ground.
- ☐ Result: Input voltage should be 7.4V +/- 0.1V

## **Device Tests:**

### **1. DRV8235RTER (Coil Driver)**

- ☐ (If needed) Switch PERI\_3V3 to the ground, the driver should be in low-power sleep mode.
- ☐ IPROPI should increase and decrease according to COIL\_P and COIL\_N.
- ☐ Write circuitpython script to establish I2C connection. Script should not return errors. (Detect address)

### **2. OPT4003DNPRQ1 (Light Sensor)**

- ☐ Write circuitpython script to establish I2C connection. Script should not return errors.
- ☐ Complete/Partial/Not block the sensor, should see significant increases in lux value.



### 3. LTC3130 (MPPT)

- ☐ Write circuitpython script to establish I2C connection. Script should not return errors.
- ☐ Input voltage between  $V_{in}$  and Ground should be at least higher than 10V as a result of the MPPT.
- ☐ Ideally, the input voltage between  $V_{in}$  and Ground should be about 16V as a result of the MPPT.
- ☐ Output voltage between  $V_{out}$  and Ground should be higher than 7.4V as a result of FB.

### Solar Cell Tests:

1.

# **-Z Board:**

## **Pre-test procedure:**

- ☐ Connect with Mainboard with J1.
- ☐ The mainboard should also connect to the Batteryboard and follow the pre-test procedure of the Batteryboard.
- ☐ Tying the fishing line on the burn wires.

## **Power Tests:**

### **1. DRV8235RTER (Coil Driver)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply.
- ☐ Measure output voltage on DRV8235RTER using a multimeter in voltage mode across the capacitor (C10/C9)
- ☐ Result: Input voltage should be 7.4V +/- 0.1V

### **2. OPT4003DNPRQ1 (Light Sensor)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply.

- ☐ Measure input voltage on OPT4003DNPRQ1 using a multimeter in voltage mode across the capacitor (C5).
- ☐ Result: Input voltage should be 3.3V +/- 0.05V

### **3. PCA9633DP2 (Burn Wire Controller)**

- ☐ Measure input voltage on PCA9633DP2 using a multimeter in voltage mode across the capacitor (C13)
- ☐ Result: Input voltage should be 3.3V +/- 0.05V

### **4. IM11DGR (Power Relay)**

- ☐ Measure input voltage on IM11DGR using a multimeter in voltage mode crossing C16.
- ☐ Result: Input voltage should be 3.3V +/- 0.05V
- ☐ Measure load on IM11DGR Pin 4 and Pin 5 using a multimeter in voltage mode.
- ☐ Result: The outcome should be 7.4V +/- 0.1V

## **Device Tests:**

### **1. DRV8235RTER (Coil Driver)**

- ☐ (If needed) Switch PERI\_3V3 to the ground, the driver should be in low-power sleep mode.

- ☐ IPROPI should increase and decrease according to COIL\_P and COIL\_N.
- ☐ Write circuitpython script to establish I2C connection. Script should not return errors. (Detect address)

## **2. OPT4003DNPRQ1 (Light Sensor)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V ( $V_{sys}$ ) to battery terminals using a DC power supply.
- ☐ Measure input voltage on OPT4003DNPRQ1 using a multimeter in voltage mode across the capacitor (C5).
- ☐ Result: Input voltage should be 3.3V +/- 0.05V

## **3. PCA9633DP2 (Burn Wire Controller)**

- ☐ Write circuitpython script to establish I2C connection. Script should not return errors. (Detect address)
- ☐ By soldering or desoldering R11, R12, R13, and R37, the detected address should change according to the datasheet.
- ☐ Write circuitpython script to manipulate the output of LED0 to LED3 pins.

- ☐ The signal output from LED0 to LED3 should correspond to circuitpython code.

#### **4. IM11DGR (Power Relay)**

- ☐ When the BURN\_RELAY\_A signal from LED3 pins of PCA9633DP2 is high, the switch shall move to pin4, driving VBURN\_A\_IN high.
- ☐

#### **5. Burn Wire**

- ☐ While the VBURN\_A\_IN is high, if the BURN\_EN is low, the corresponding burn wire should be heated.
- ☐ Once the burn wire increases temperature, the fishing line should melt.

#### **~~6. DXW21HN5011BL (Transformer)~~**

#### **~~7. CGGBP.18.4.A.02 (GPS Antenna)~~**

### **+Z Board:**

#### **Pre-test procedure:**

- ☐ Mount all four sun sensor micro PCBs on each edge at 45 degrees.
- ☐ Connect with Mainboard with J1.
- ☐ The mainboard should also connect to the Batteryboard and follow the pre-test procedure of the Batteryboard.

## **Power Tests:**

### **1. DRV8235RTER (Coil Driver)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V (V<sub>sys</sub>) to battery terminals using a DC power supply.
- ☐ Measure output voltage on DRV8235RTER using a multimeter in voltage mode across the capacitor (C11/C12)
- ☐ Result: Input voltage should be 7.4V +/- 0.1V

### **2. Micro PCBs (Sun Sensors)**

- ☐ If the Solar Panel cannot support itself or sunlight isn't available, apply 7.4V (V<sub>sys</sub>) to battery terminals using a DC power supply.
- ☐ Measure output voltage on Micro PCBs using a multimeter in voltage mode across the capacitor (C8/C5/C6/C7).

- ☐ Result: Input voltage should be 3.3V +/- 0.05V

### **3. LTC3130 (MPPT)**

- ☐ Measure the voltage generated ( $V_{in}$ ) from the deployable using a multimeter in voltage mode across the capacitor (C18-C21).
- ☐ Input voltage between  $V_{in}$  and Ground should be at least higher than 10V as a result of the MPPT.
- ☐ Ideally, the input voltage between  $V_{in}$  and Ground should be about 16V as a result of the MPPT.
- ☐ Output voltage between  $V_{out}$  and Ground should be higher than 7.4V as a result of FB.

### **4. LTC4412xS6 (Or-ing)**

- ☐ Measure the voltage using a multimeter in voltage mode across the capacitor (C10).
- ☐ Result: Input voltage should be ?V +/- ?V

### **5. ADM1176-1ARMZ-R7 (Power Monitor)**

- ☐ Measure the voltage using a multimeter in voltage mode between R55 and the Ground.
- ☐ Result: Input voltage should be 7.4V +/- 0.1V

## Device Tests:

### 1. DRV8235RTER (Coil Driver)

- ☐ (If needed) Switch PERI\_3V3 to the ground, the driver should be in low-power sleep mode.
- ☐ IPROPI should increase and decrease according to COIL\_P and COIL\_N.
- ☐ Write circuitpython script to establish I2C connection. Script should not return errors. (Detect address)

### 2. Micro PCBs (Sun Sensors)

- ☐ Write circuitpython script to establish I2C connection. Script should not return errors.
- ☐ Complete/Partial/Not block the sensor, should see significant increases in lux value.

### 3. LTC3130 (MPPT)

- ☐ Write circuitpython script to establish I2C connection. Script should not return errors.
- ☐ Input voltage between Vin and Ground should be at least higher than 10V as a result of the MPPT.



- ☐ Ideally, the input voltage between  $V_{in}$  and Ground should be about 16V as a result of the MPPC.
- ☐ Output voltage between  $V_{out}$  and Ground should be higher than 7.4V as a result of FB.

## **Solar Cell Tests:**

1.

